 


LAB 3

Shantanu Singh – 1005218514


Part I




2. Write the Verilog Code for the 7 – to – 1 MUX.

Ans – Please check the `sevento1.v` file attached with this file

3. Attach a screenshot of the simulation

 


Part II

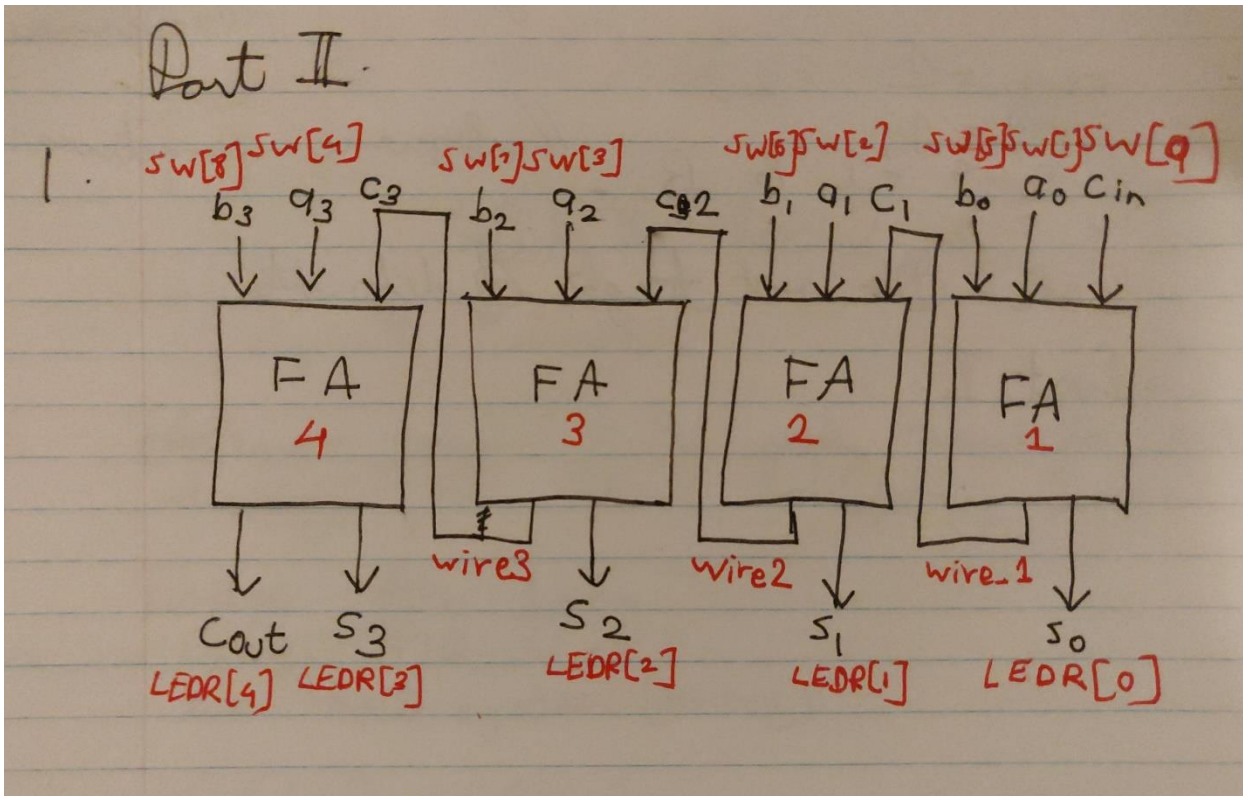

2. Write the Verilog Code for Full – Adder.


Ans – Please check the fulladder4.v file uploaded with this.

3. Attach a screenshot of the simulation

 

Part III

1.

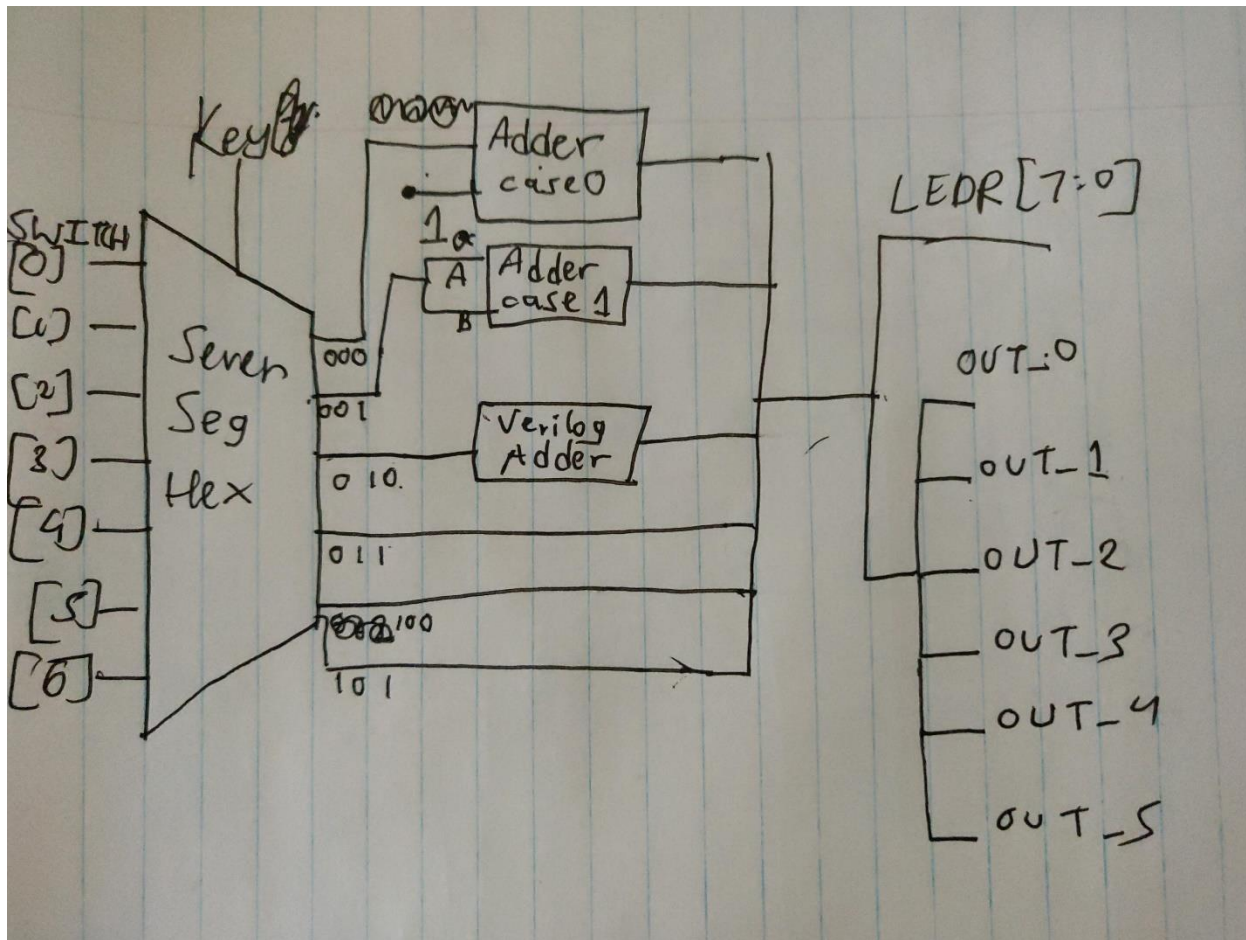

2. Write the Verilog Code for the ALU

Ans – Please check ALU.v attached with this file

3. Attach a screenshot of the simulation

