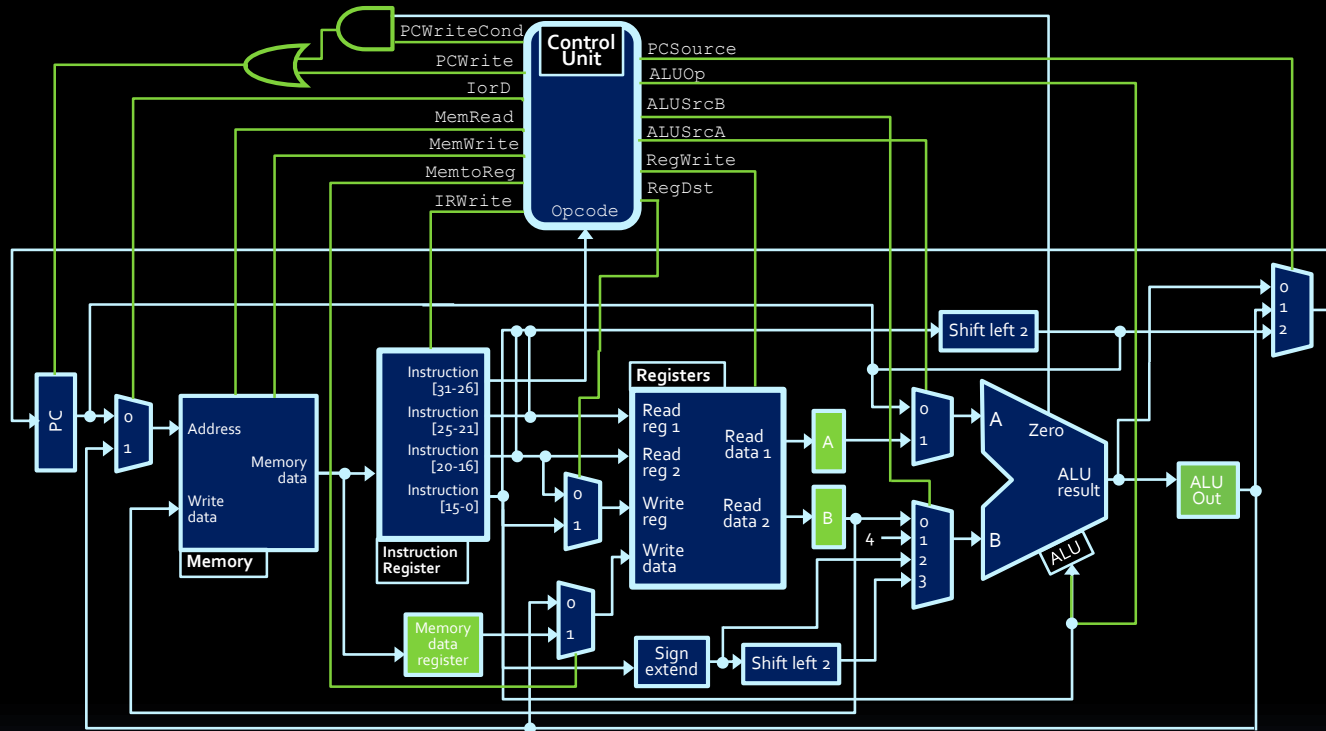




Week 9 Review



Question #1




- Given the datapath above, what signals would the control unit turn on and off in order to add \$t1 to \$t2 and store the result in \$t7?

Basic approach


1. Figure out the **data source(s)** and **destination**.
2. Determine the **path** of the data.
3. Deduce the **signal values** that cause this path:
 - a) Start with `Read & Write` signals (at most one can be high at a time).
 - b) Then, mux signals along the data path.
 - c) Non-essential signals get an `X` value.

Question #1 (cont'd)

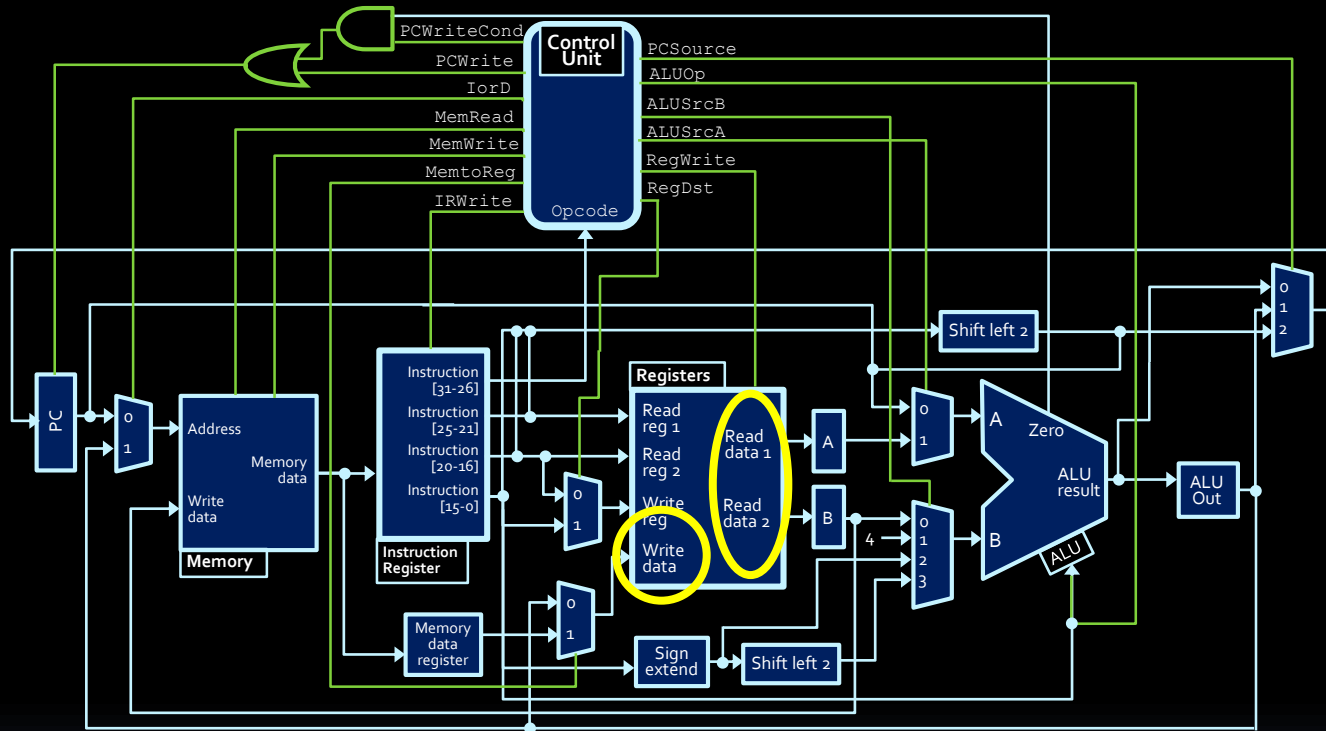


- Step #1: Data source and destination
 - Data starts in register block.
 - Data goes to register block.

Question #1 (cont'd)

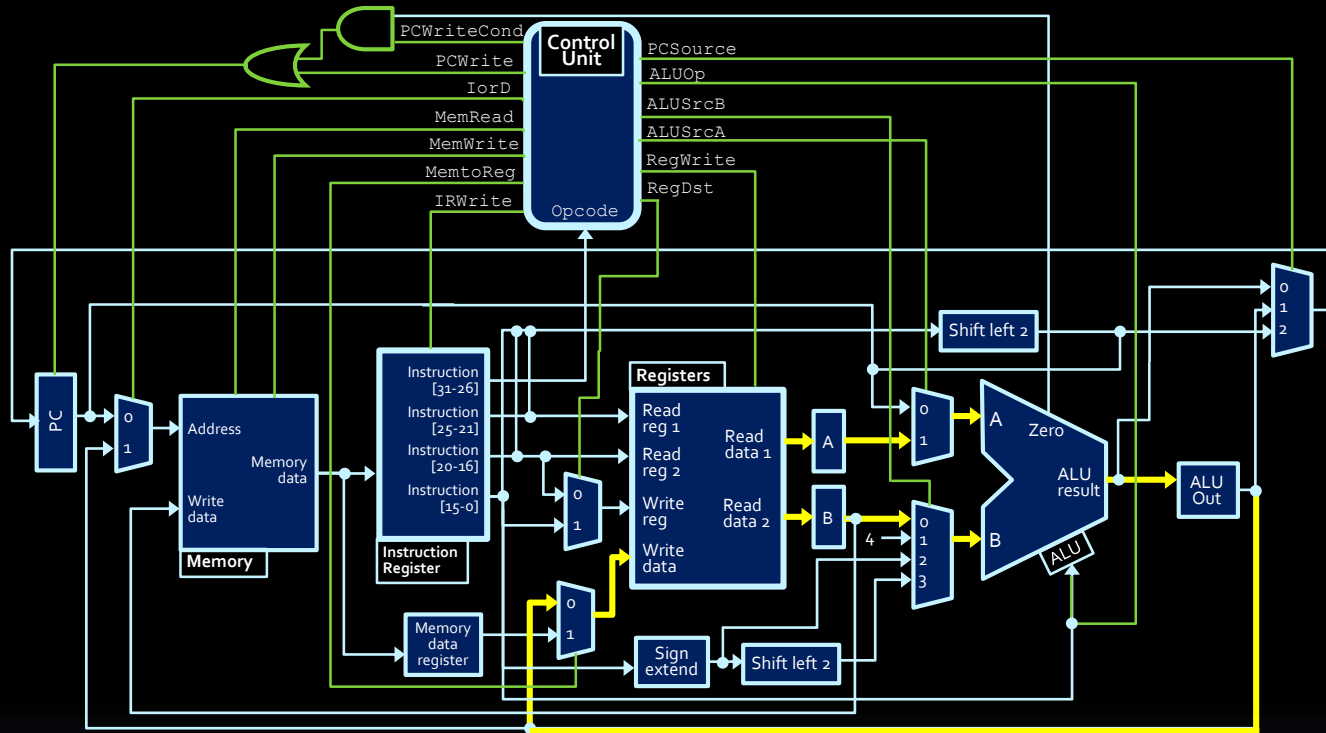

- Step #2: Determine the path of the data
 - Data needs to go through the ALU before heading back into the register file.


Question #1 (cont'd)

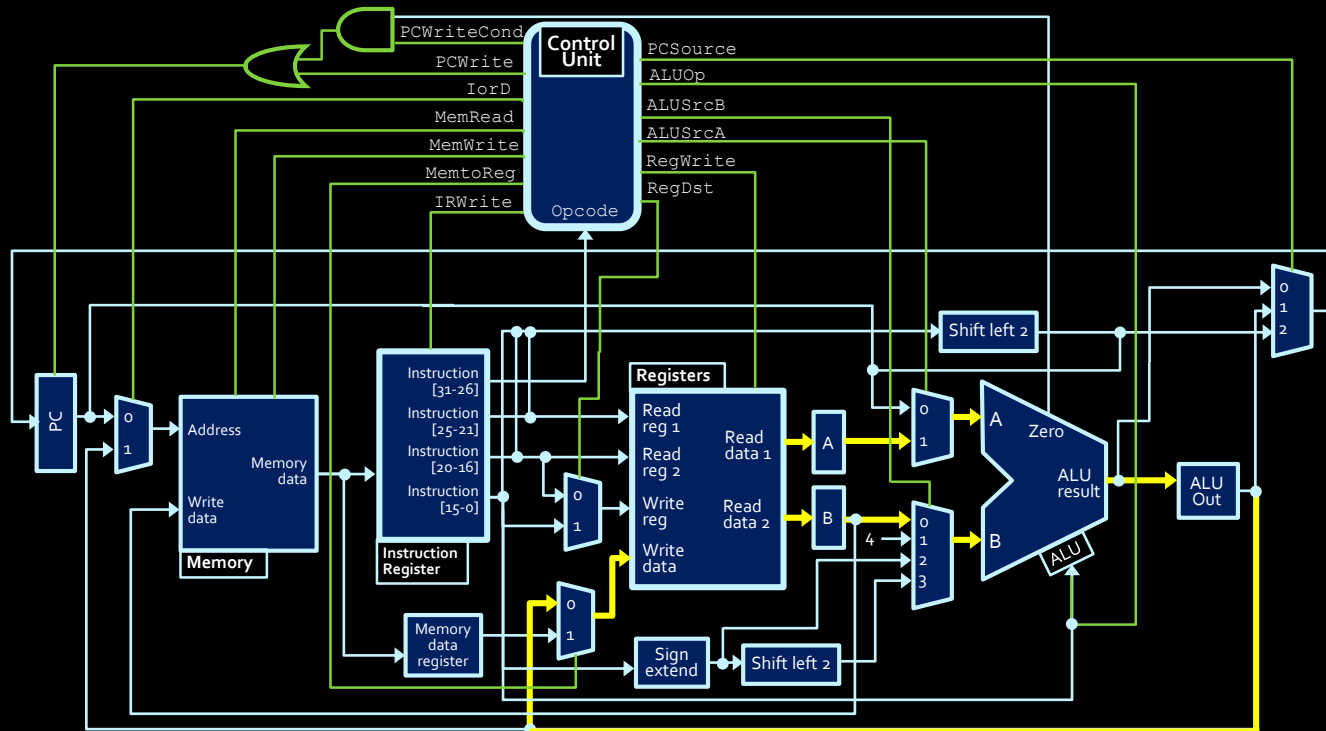

■ Step #3a: Read & Write signals

- Only RegWrite needs to be high.
- PCWrite, PCWriteCond, MemRead, MemWrite, IRWrite would be low.


Question #1 (cont'd)

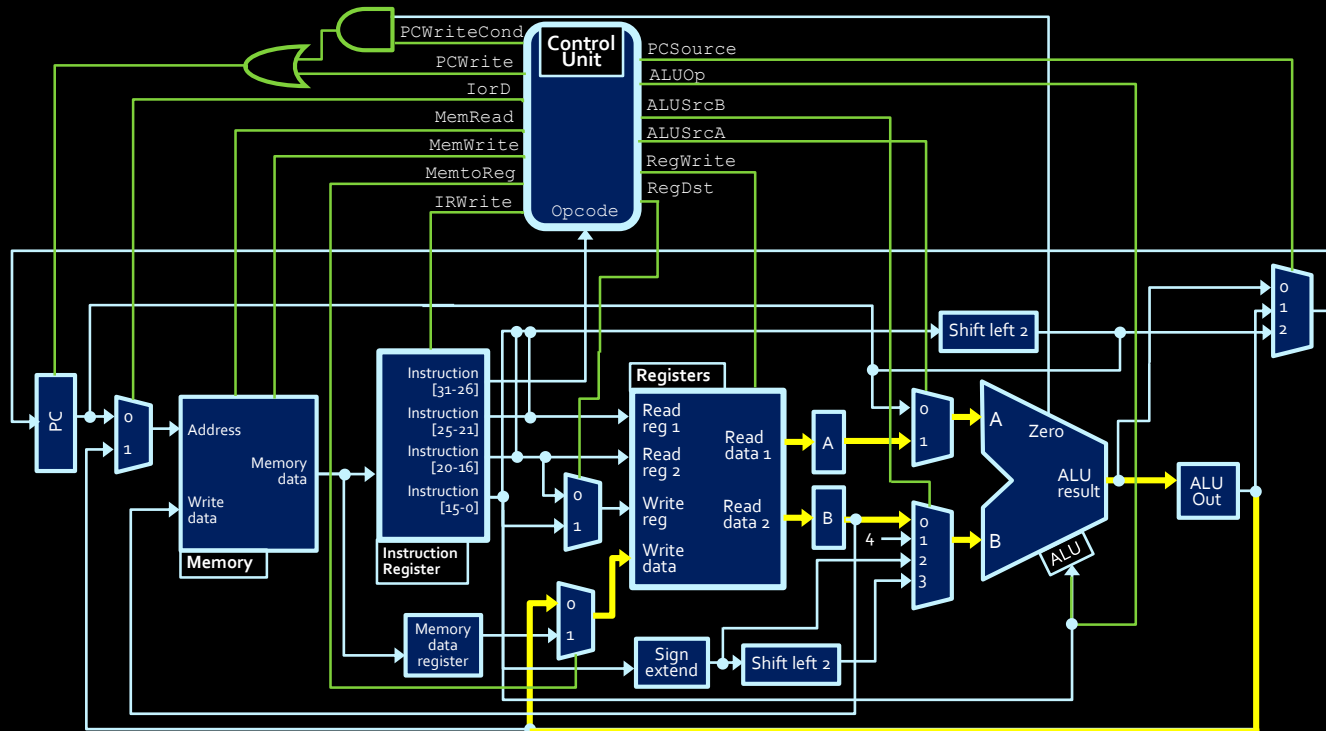

■ Step #3b: Data path signals

- Muxes before ALU: $ALUSrcA \rightarrow 1, ALUSrcB \rightarrow 00$.
- $ALUOp \rightarrow 001$ (Add)
- Mux before registers: $MemToReg \rightarrow 0$

Question #1 (cont'd)

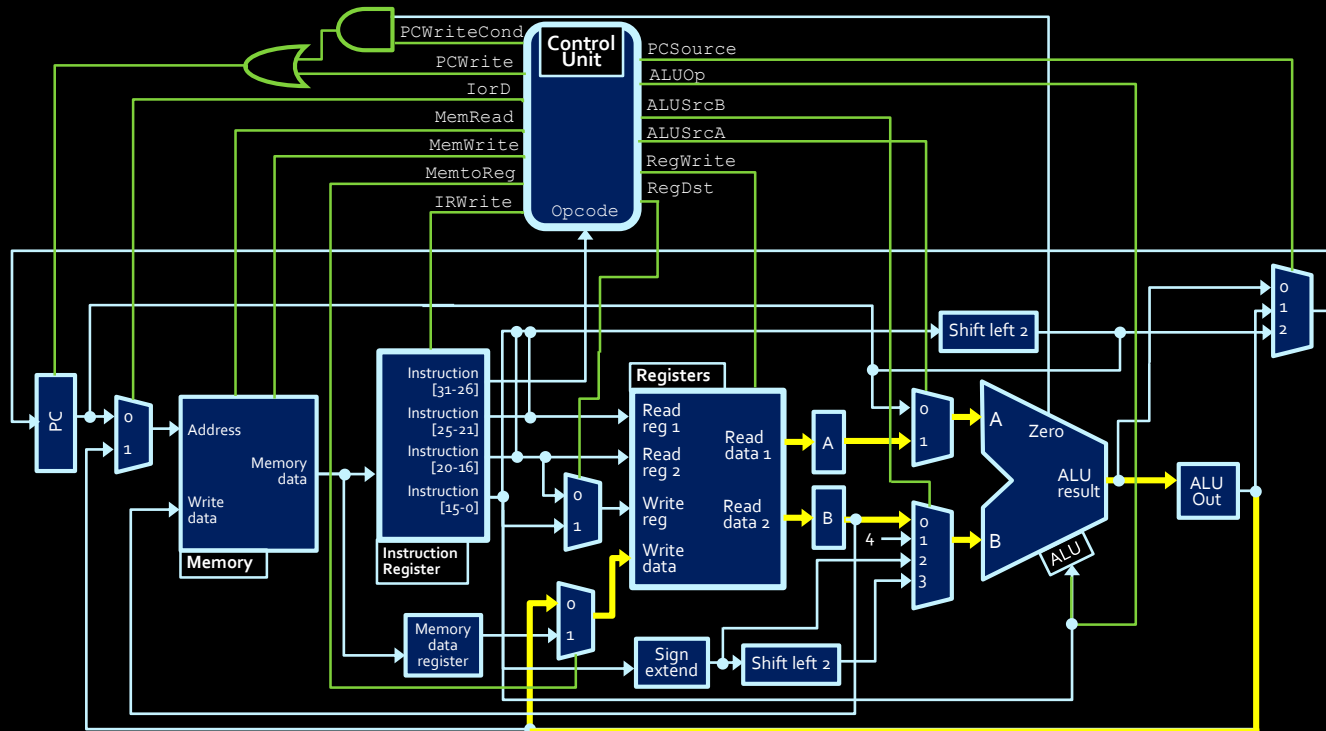


- Step #3c: Non-essential signals
 - No writing to PC: `PCSource` → X.
 - No reading from memory: `IorD` → X.

Question #1 (cont'd)


- `PCWrite = 0`
 - `PCWriteCond = 0`
 - `IorD = X`
 - `MemRead = 0`
 - `MemWrite = 0`
 - `MemToReg = 0`
 - `IRWrite = 0`
 - `PCSource = X`
 - `ALUOp = 001`
 - `ALUSrcA = 1`
 - `ALUSrcB = 00`
 - `RegWrite = 1`
 - `RegDst = 1`
- Note: `RegDst` rule
 - high for 3-register operations
 - low for 2-register operations

Question #2

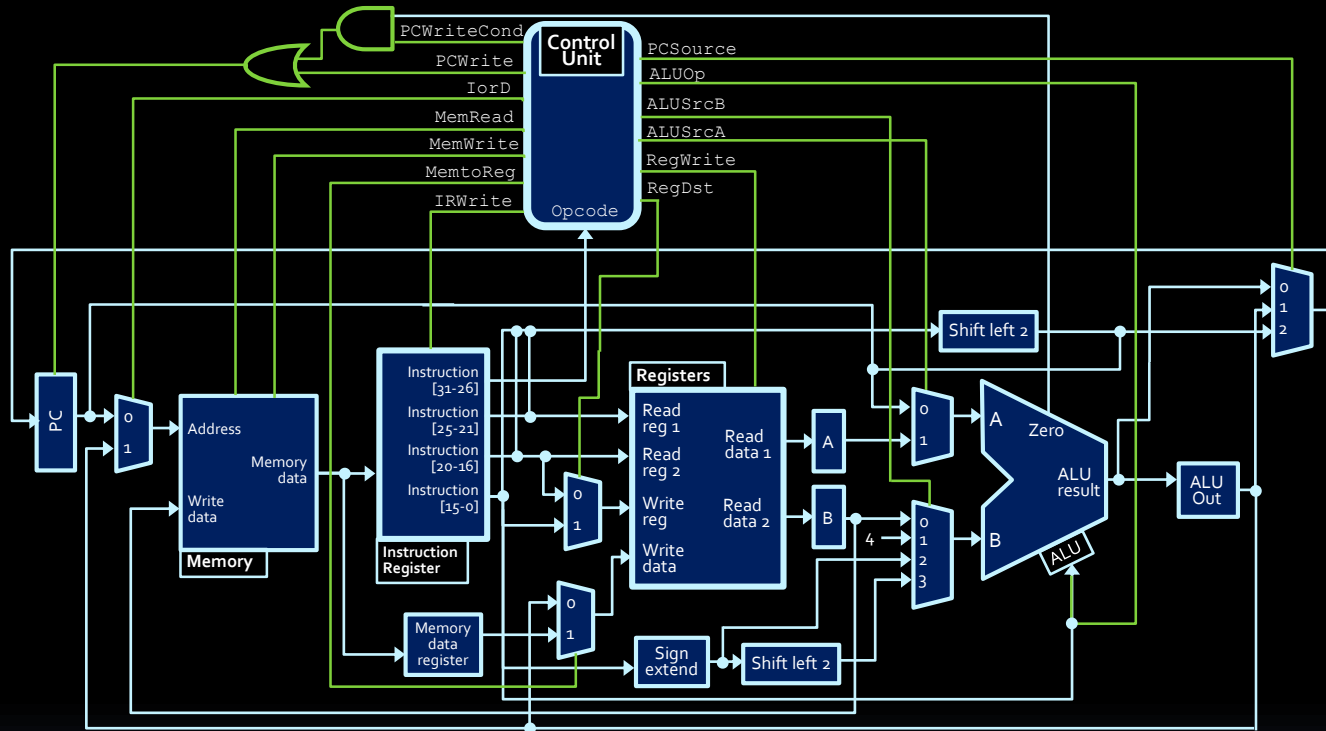


- Given the datapath above, what signals would the control unit turn on and off in order to branch to 100 instructions forward (add 100×4 to the program counter)?

Question #2

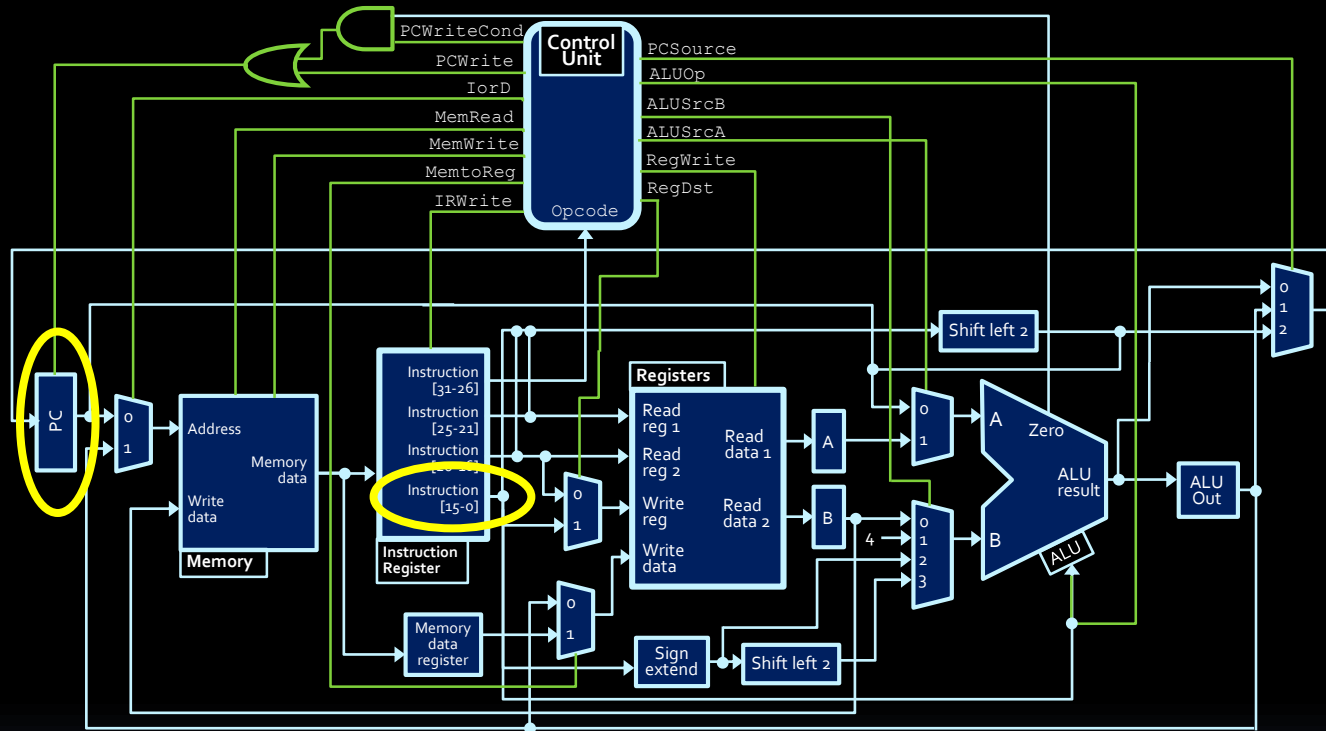

- Step #1: Source and destination.
 - Program counter is both source and destination.
 - Immediate value from instruction is other source.

Question #2

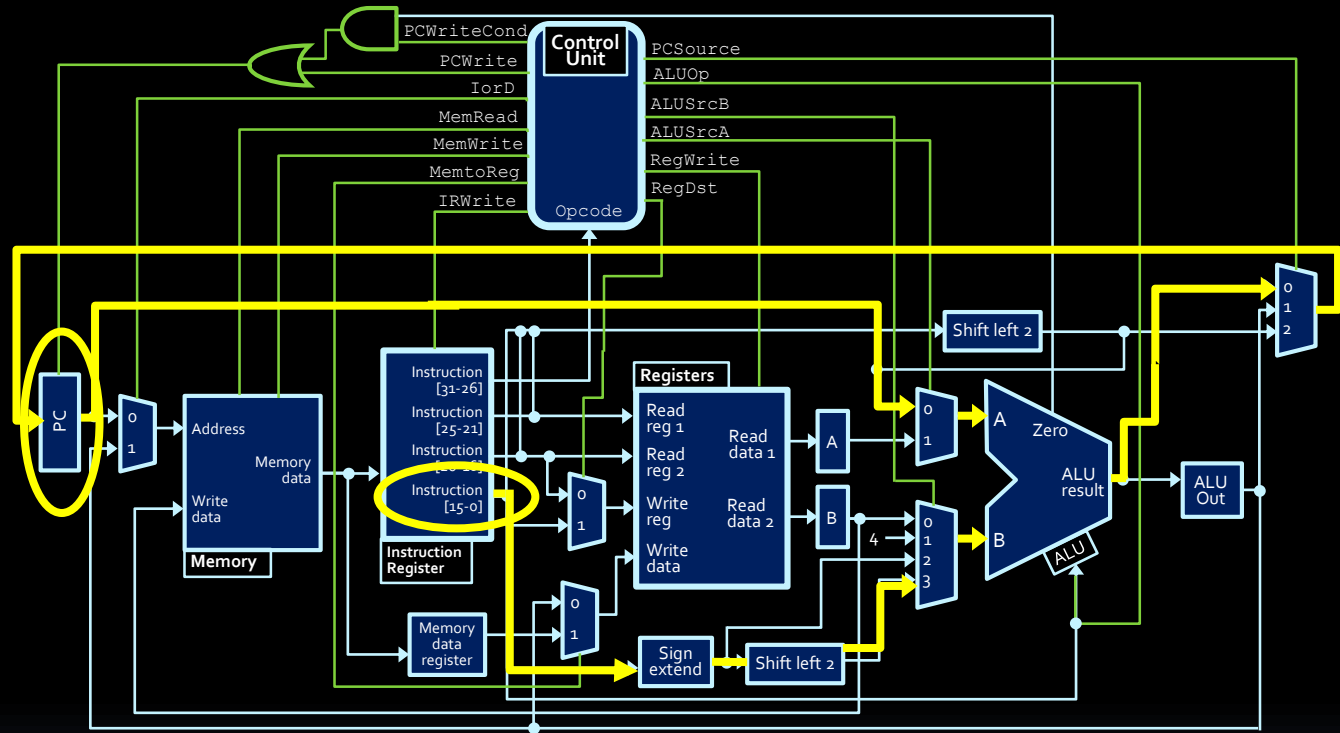

- Step #2: Path between source and destination.

Question #2 (cont'd)

- **Read / Write signals:**

- PCWrite high, all others low.
 - PCWriteCond is X, when PCWrite is high.

- **Datapath signals:**

- ALUSrcA \rightarrow 0
- ALUSrcB \rightarrow 3 (100 is an immediate value; needs to come from the instruction, and needs to be word-aligned because it concerns 4-byte instructions.)
- PCSource \rightarrow 0


- **Non-essential signals:**

- IorD, MemToReg, RegDst

Question #2 (cont'd)

- `PCWrite = 1`
- `PCWriteCond = X`
- `IorD = X`
- `MemRead = 0`
- `MemWrite = 0`
- `MemToReg = X`
- `IRWrite = 0`
- `PCSource = 0`
- `ALUOp = 001`
- `ALUSrcA = 0`
- `ALUSrcB = 11`
- `RegWrite = 0`
- `RegDst = X`

Question #3

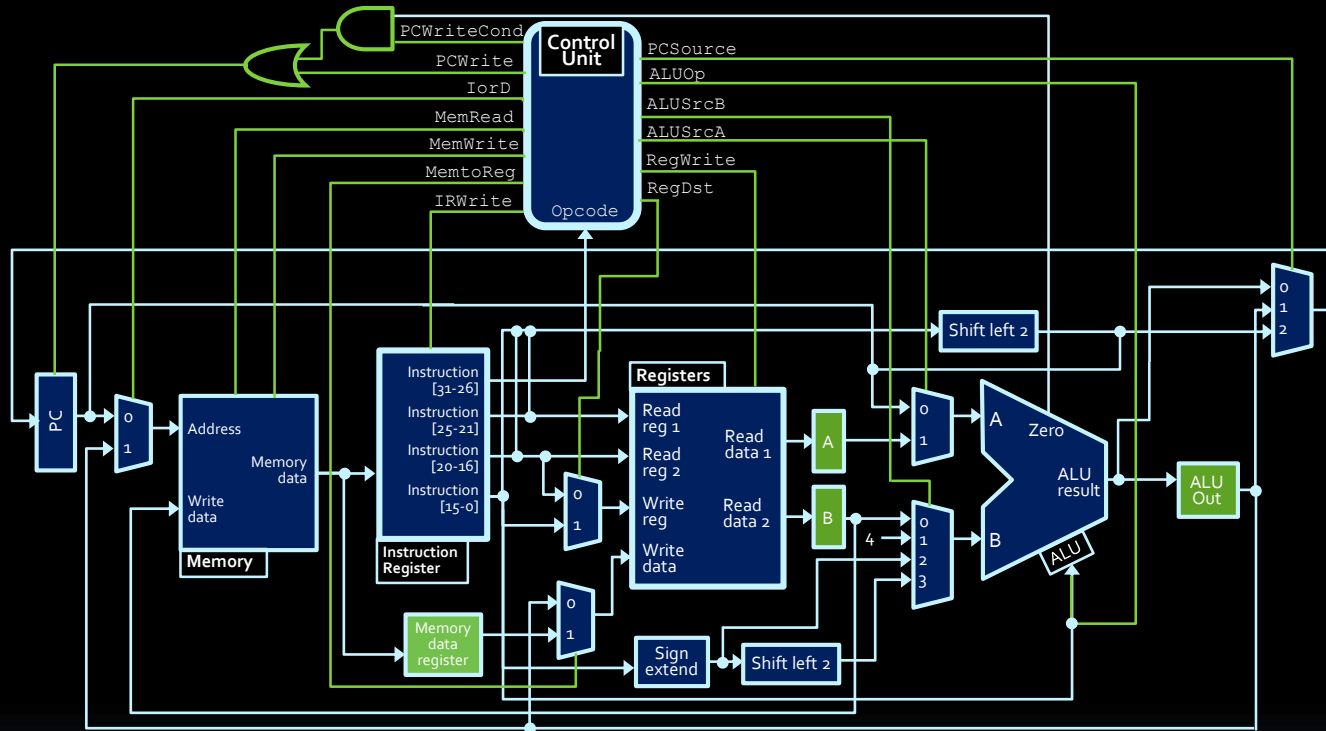

- Given the datapath above, what signals would the control unit turn on and off in order to load a memory value into $\$t0$?
- Note: Assumes that the address of this memory location has already been computed and sent to the memory address input.

1000000



- 16

Question #3 (cont'd)

- **Read / Write signals:**
 - RegWrite and MemRead high, all others low.
- **Datapath signals:**
 - MemToReg \rightarrow 1
 - RegDst \rightarrow 0
- **Non-essential signals:**
 - IorD, PCSource, AluSrcA, AluSrcB

Question #3 (cont'd)

- PCWrite = 0
- PCWriteCond = 0
- IorD = X
- MemRead = 1
- MemWrite = 0
- MemToReg = 1
- IRWrite = 0
- PCSource = X
- ALUOp = XXX
- ALUSrcA = X
- ALUSrcB = XX
- RegWrite = 1
- RegDst = 0

Now do the same question, but for entire execution phase of `lw $t0, 10($t1)` instruction; i.e. Produce the address for memory as well.

Note: The highlighted signals cannot be left “don’t care” now.

Question #4

- What are the following assembly language instructions doing?

```
sub $t7, $t0, $t1
```



Subtract register \$t1 from \$t0 and placing the result into \$t7

```
andi $t7, $t0, 15
```



Bitwise AND between register \$t0 and 15 (1111), **NOTE ZE**, with the result placed into register \$t7

```
sra $t2, $t1, 2
```




Arithmetic shift of register \$t1 two bits to the right, with the result stored in \$t2

Question #5

- How do you translate the following assembly language instruction into machine code?

```
add $t7, $t0, $t1
```

R-type instruction!

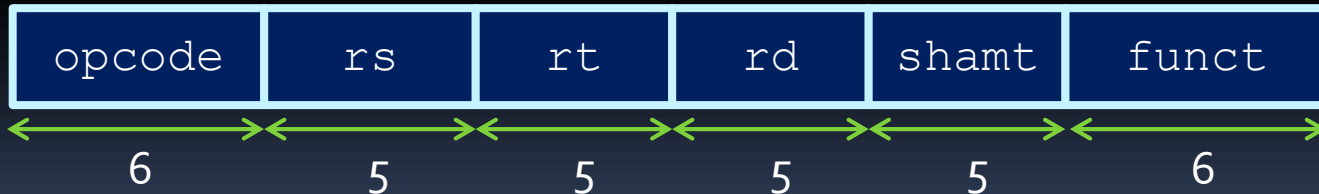

Question #5

```
add $t7, $t0, $t1
```

■ Step #1: The opcode

- Arithmetic operations start with six 0's, and have the function identifier at the end.

```
000000 sssss ttttt dddd XXXXX 100000
```

■ Step #2: The register numbers

- Remember that \$t0 does not translate to register 0
- The temporary registers start at register 8, so \$t0 → 8, \$t1 → 9 and \$t7 → 15

```
000000 01000 01001 01111 XXXXX 100000
```

