




Week 6 Lectorial



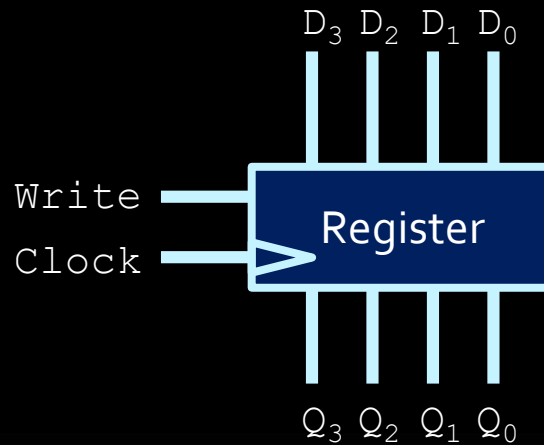Question #1


- Imagine you have access to a 4-bit register.



- What does the `Write` signal do?

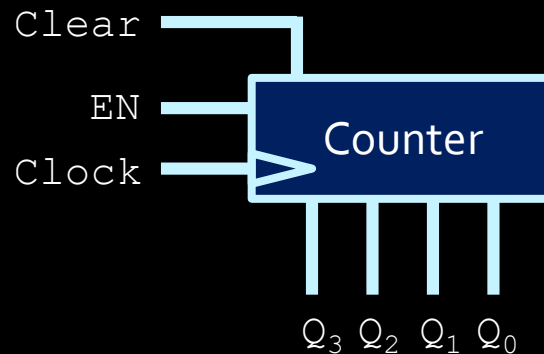Question #2


- Assume that you have access to a counter circuit:



- How do you make a signal that goes high after 10 clock cycles?
- How do you make a signal that goes high every 10 clock cycles?

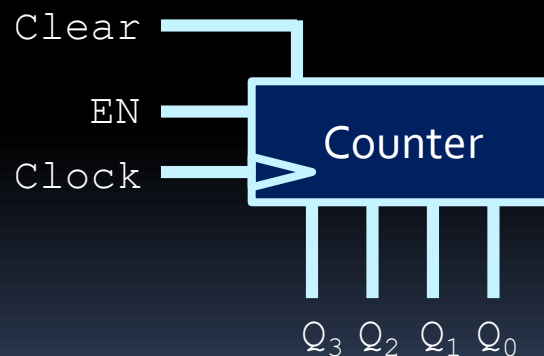Question #2 (cont'd)

- How do you make a signal that goes high every 100 clock cycles, only using 4-bit counters like the one below (and a few additional gates)?



Question #3

- How many flip-flops would you need to implement the following finite state machine (FSM)?

- 11 states
- # flip-flops = $\lceil \log_2 (\# \text{ of states}) \rceil$
- # flip-flops = 4





Reminder: How to Design FSM

- As a brief reminder:
 1. Draw state diagram
 2. Derive state table from state diagram
 3. Assign flip-flop configuration to each state
 - Number of flip-flops needed is: $\lceil \log(\# \text{ of states}) \rceil$
 4. Redraw state table with flip-flop values
 5. Derive combinational circuit for output and for each flip-flop input.


Review of FSMs

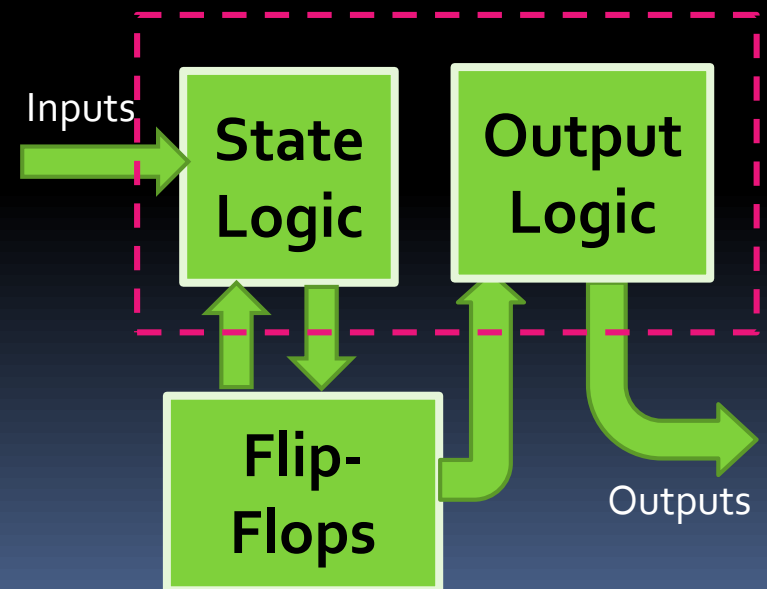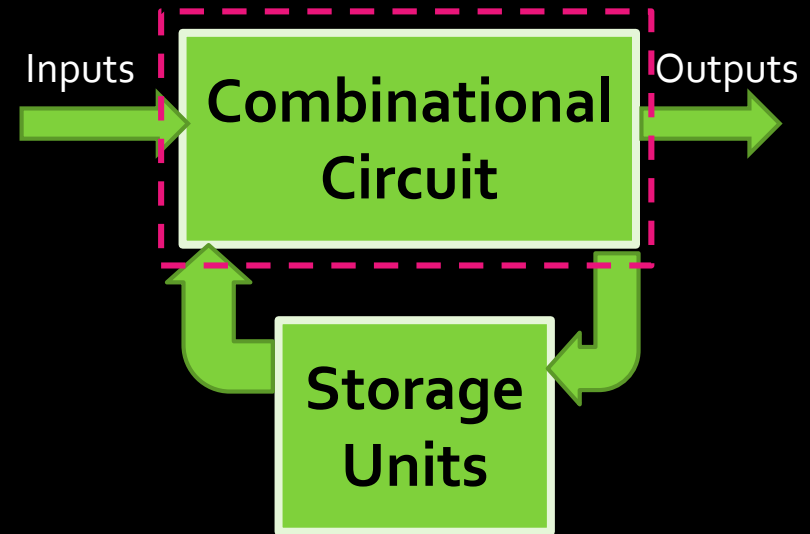- Step 5 requires two combinational circuit design tasks.
 - For **Moore machines** (pictured bottom right), output is determined solely based on current state (i.e. flip-flop values).



Review of FSMs

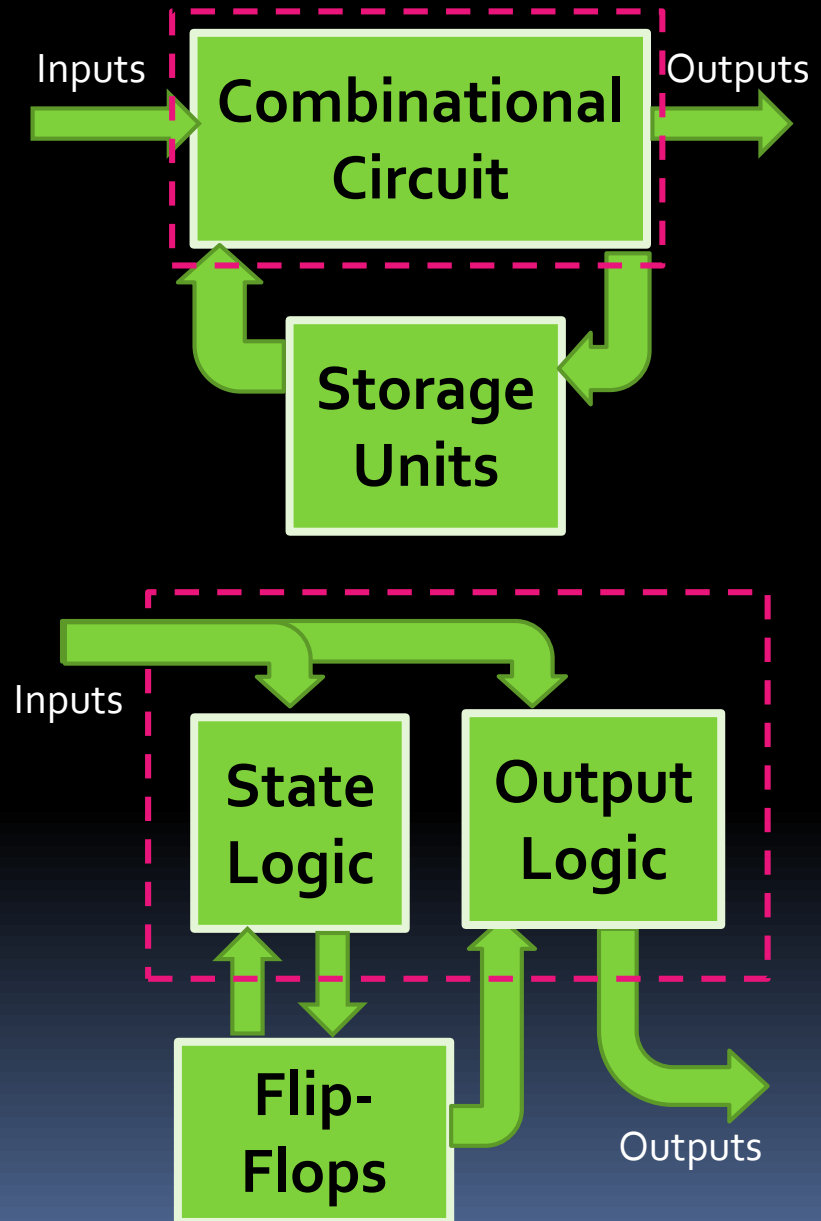
- For **Mealy machines**, output is determined by both the current state and the current input values.
 - For simplicity, most of our examples will focus on Moore machines.




State diagrams with output

- Output values are incorporated into the state diagram, depending on the machine used.

➤ Moore Machine

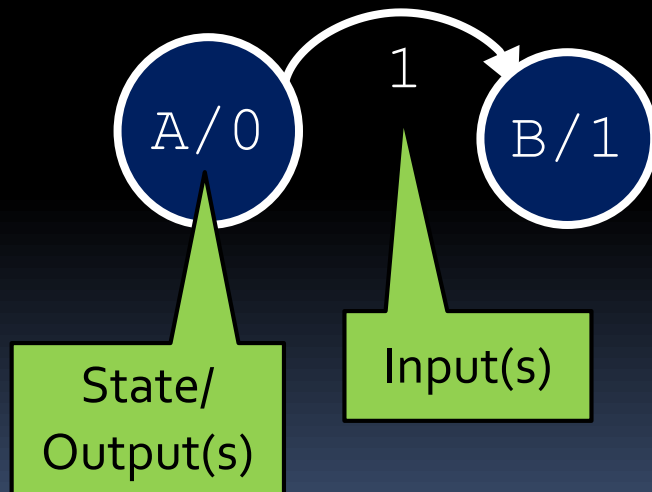

➤ Mealy Machine

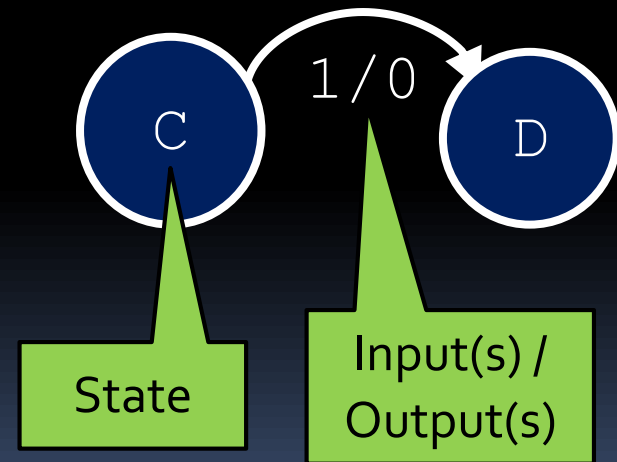


FSM Example: Barcode Reader

- When scanning UPC barcodes, the laser scanner looks for black and white bars that indicate the start of the code.
- If black is read as a 1 and white is read as a 0, the start of the code (from either direction) has a 1010 pattern.
 - Can you create a state machine that detects this pattern?



Step #1: Draw state diagram

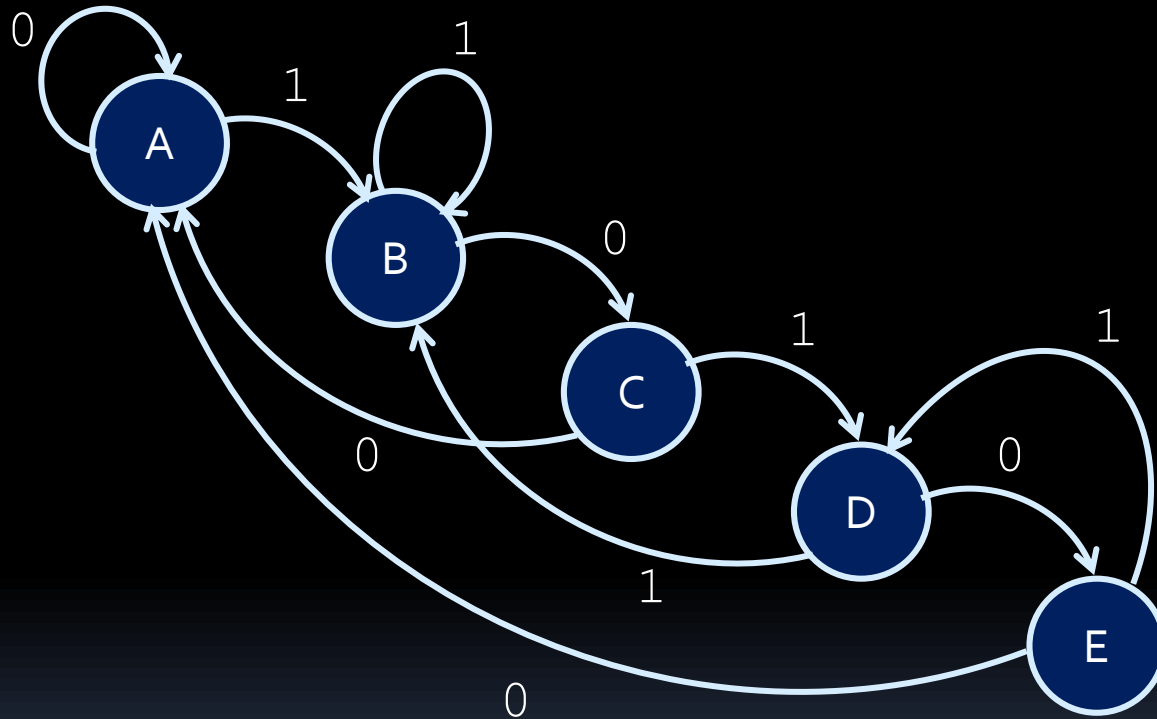

Step #2: State Table

- Output Z is determined by the current state.
 - Denotes Moore machine.
- Next step: allocate flip-flops values to each state.
 - How many flip-flops will we need for 5 states?
 - Recall:
 - $\# \text{ flip-flops} = \lceil \log(\# \text{ of states}) \rceil$


Present State	Z	x	Next State
A	0	0	A
A	0	1	B
B	0	0	C
B	0	1	B
C	0	0	A
C	0	1	D
D	0	0	E
D	0	1	B
E	1	0	A
E	1	1	D

Step #3: Flip-Flop Assignment

- 3 flip-flops needed here.
- Assign states carefully though!
- Can't simply do this:

➤ A = 100 ➤ B = 011
➤ C = 010 ➤ D = 001
➤ E = 000

Why not?

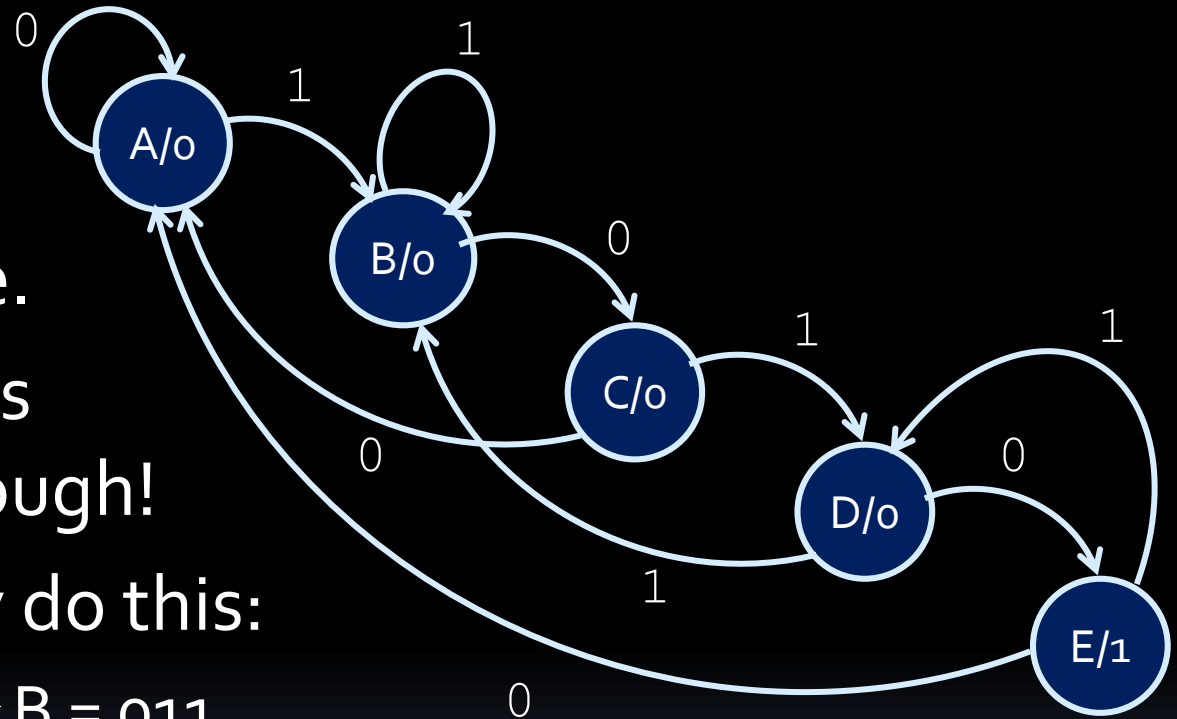


Step #3: Flip-Flop Assignment

- Be careful of **race conditions**.

- Better solution:

➤ A = 000 ➤ B = 001
➤ C = 011 ➤ D = 101
➤ E = 100

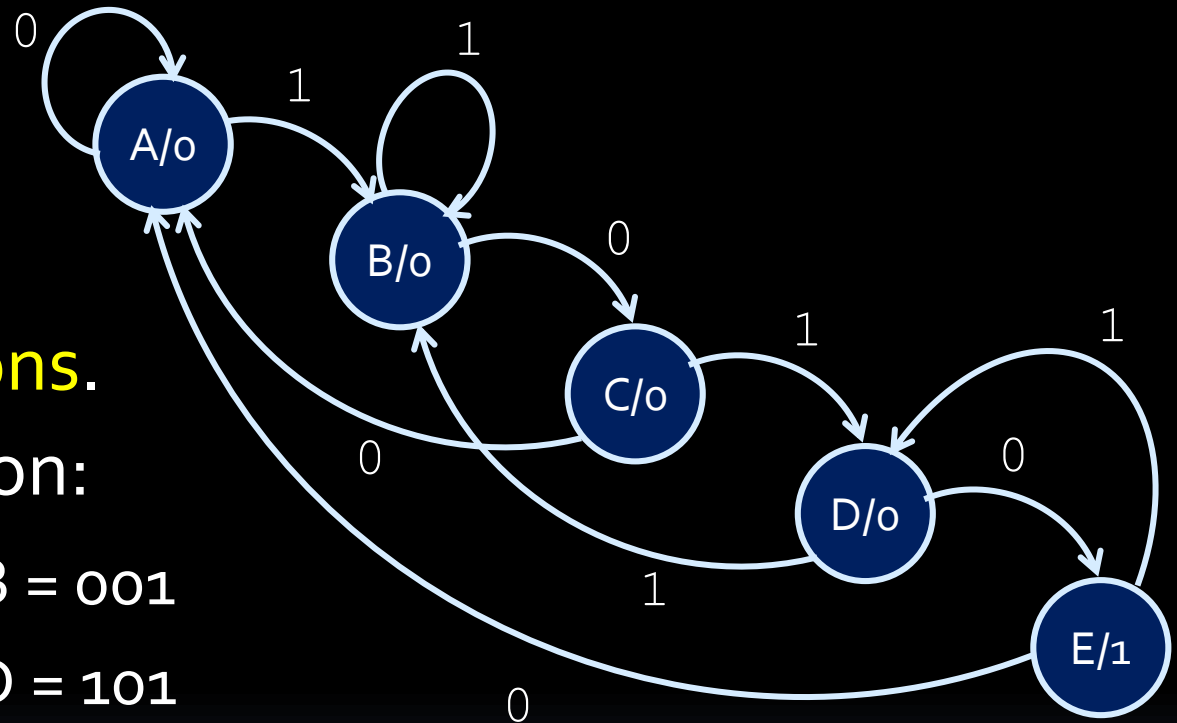- Does it still have race conditions?(e.g. $C \rightarrow D$, or $C \rightarrow A$, or $D \rightarrow B$?)
 - Sometimes, **extra flip-flops** may be necessary.



Step #4: Redraw State Table

- From here, we can construct the K-maps for the state logic combinational circuit.
 - Derive equations for each flip-flop value, given the previous values and the input X .
 - Three equations total, plus one more for Z (trivial for Moore machines).

Present State			Z	X	Next State		
0	0	0	0	0	0	0	0
0	0	0	0	1	0	0	1
0	0	1	0	0	0	1	1
0	0	1	0	1	0	0	1
0	1	1	0	0	0	0	0
0	1	1	0	1	1	0	1
1	0	1	0	0	1	0	0
1	0	1	0	1	0	0	1
1	0	0	1	0	0	0	0
1	0	0	1	1	1	0	1

Step 5: Circuit design

- Karnaugh map for F_2 :

	$\overline{F_0} \cdot \overline{X}$	$\overline{F_0} \cdot X$	$F_0 \cdot X$	$F_0 \cdot \overline{X}$
$\overline{F_2} \cdot \overline{F_1}$	0	0	0	0
$\overline{F_2} \cdot F_1$	X	X	1	0
$F_2 \cdot F_1$	X	X	X	X
$F_2 \cdot \overline{F_1}$	0	1	0	1

$$F_2 = F_1 X + F_2 \overline{F_0} X + F_2 F_0 \overline{X}$$

Step 5: Circuit design

- Karnaugh map for F_1 :

	$\overline{F_0} \cdot \overline{X}$	$\overline{F_0} \cdot X$	$F_0 \cdot X$	$F_0 \cdot \overline{X}$
$\overline{F_2} \cdot \overline{F_1}$	0	0	0	1
$\overline{F_2} \cdot F_1$	X	X	0	0
$F_2 \cdot F_1$	X	X	X	X
$F_2 \cdot \overline{F_1}$	0	0	0	0

$$F_1 = F_2 F_1 F_0 \overline{X}$$

Step 5: Circuit design

- Karnaugh map for F_0 :

	$\overline{F_0} \cdot \overline{X}$	$\overline{F_0} \cdot X$	$F_0 \cdot X$	$F_0 \cdot \overline{X}$
$\overline{F_2} \cdot \overline{F_1}$	0	1	1	1
$\overline{F_2} \cdot F_1$	X	X	1	0
$F_2 \cdot F_1$	X	X	X	X
$F_2 \cdot \overline{F_1}$	0	1	1	0

$$F_0 = X + \overline{F_2} \overline{F_1} F_0$$

Step 5: Circuit design

- Output value Z goes high based on the following output equation:

$$Z = F_2 \overline{F_1} \overline{F_0}$$

- Note: All of these equations would be different, given different flip-flop assignments!
 - ▣ Practice alternate assignment for the midterm 😊