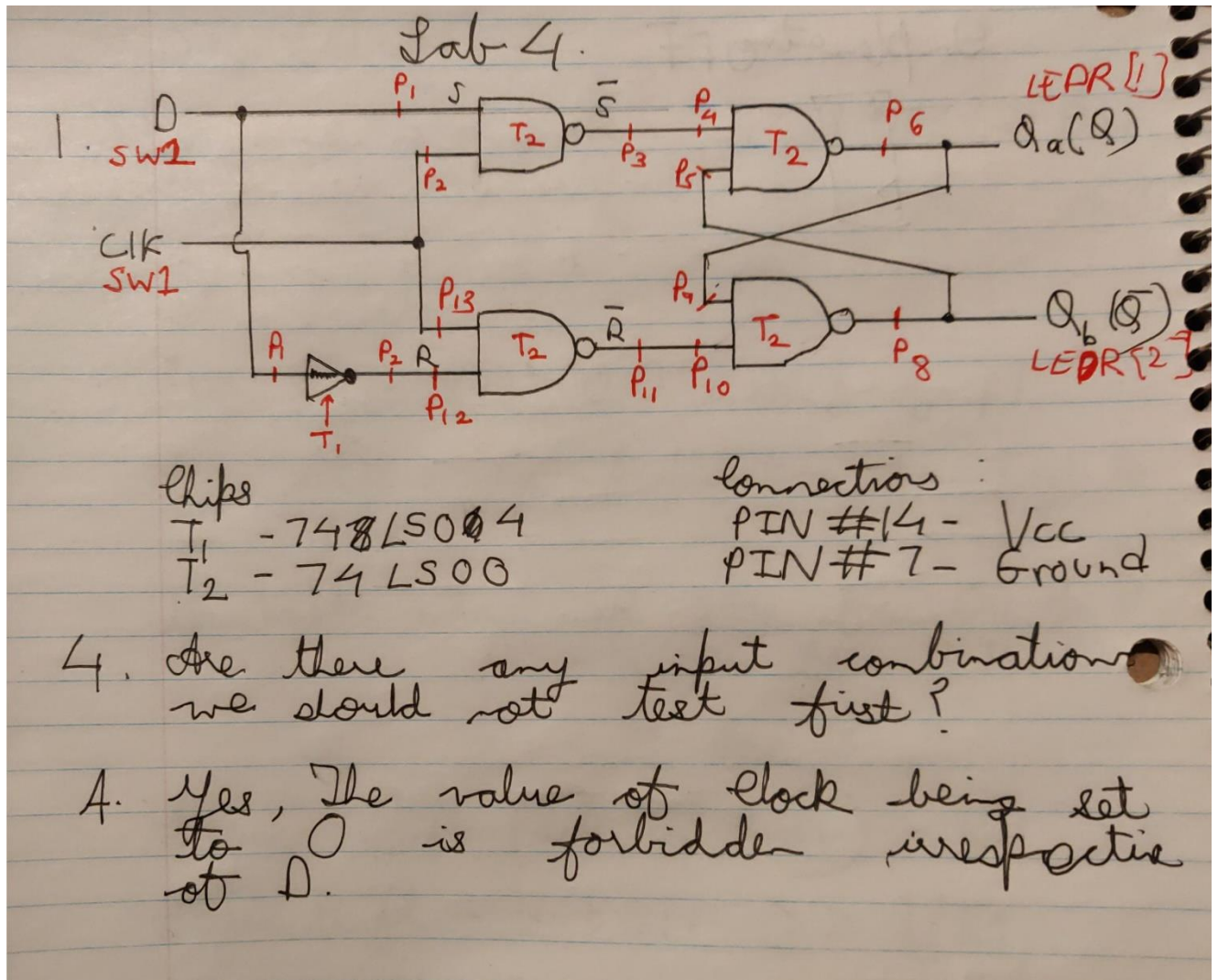



Lab 4

Part I



Part II

1. Create a Verilog Module – Please refer to `ALU_REG.v`
2. Run the simulation and Show Screenshots – Please refer to the screenshots below and `ALU_REG.do` if required.

 


Part III

1. What is the behaviour of the 8 – bit shift register shown in Figure 6?

Ans – The Multiplexer only decides the input of D and the value of the register is unchanged.

Load and ShiftRight are connect to the MUX which is connected to D so Register is constant.

2. Draw a Schematic

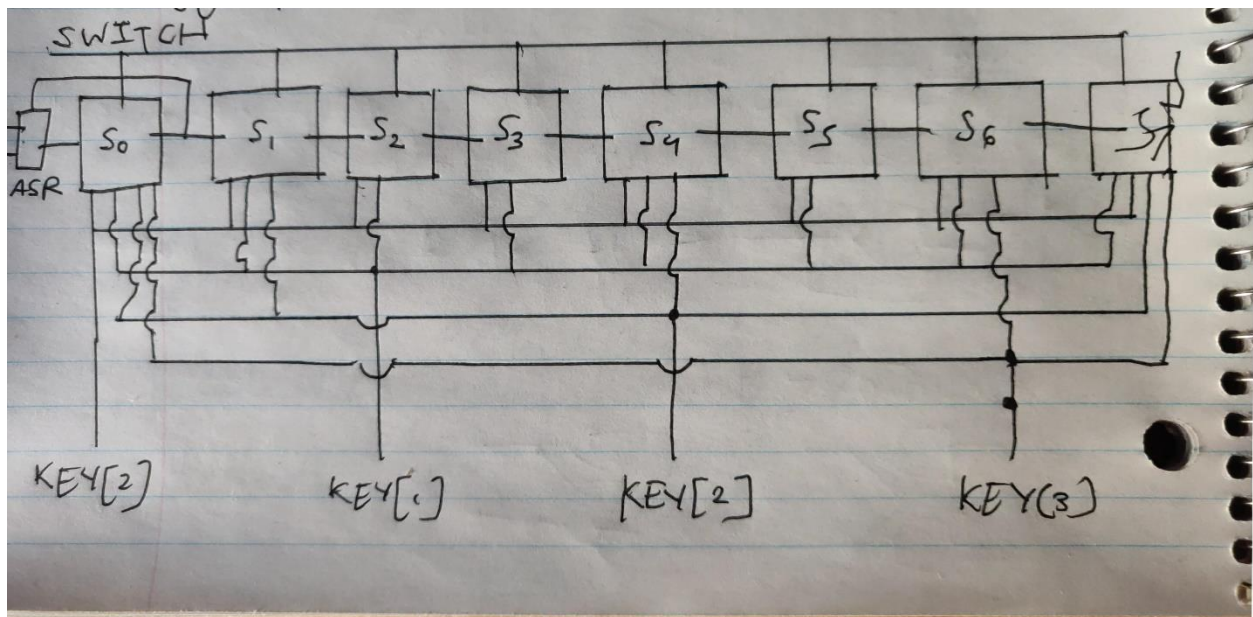

3 & 4. Please refer to *SHIFT_REG.v*

5. *Compile and Sim and attach Screenshots of the output.*

