 


CSC258 Pre – Lab 7


Part 1

9. Attach screenshot of ram32x4.v simulations





10. Instantiate `ram32x4.v` to a top – level verilog module – Please check `BRAM.v`

11. Draw a schematic –

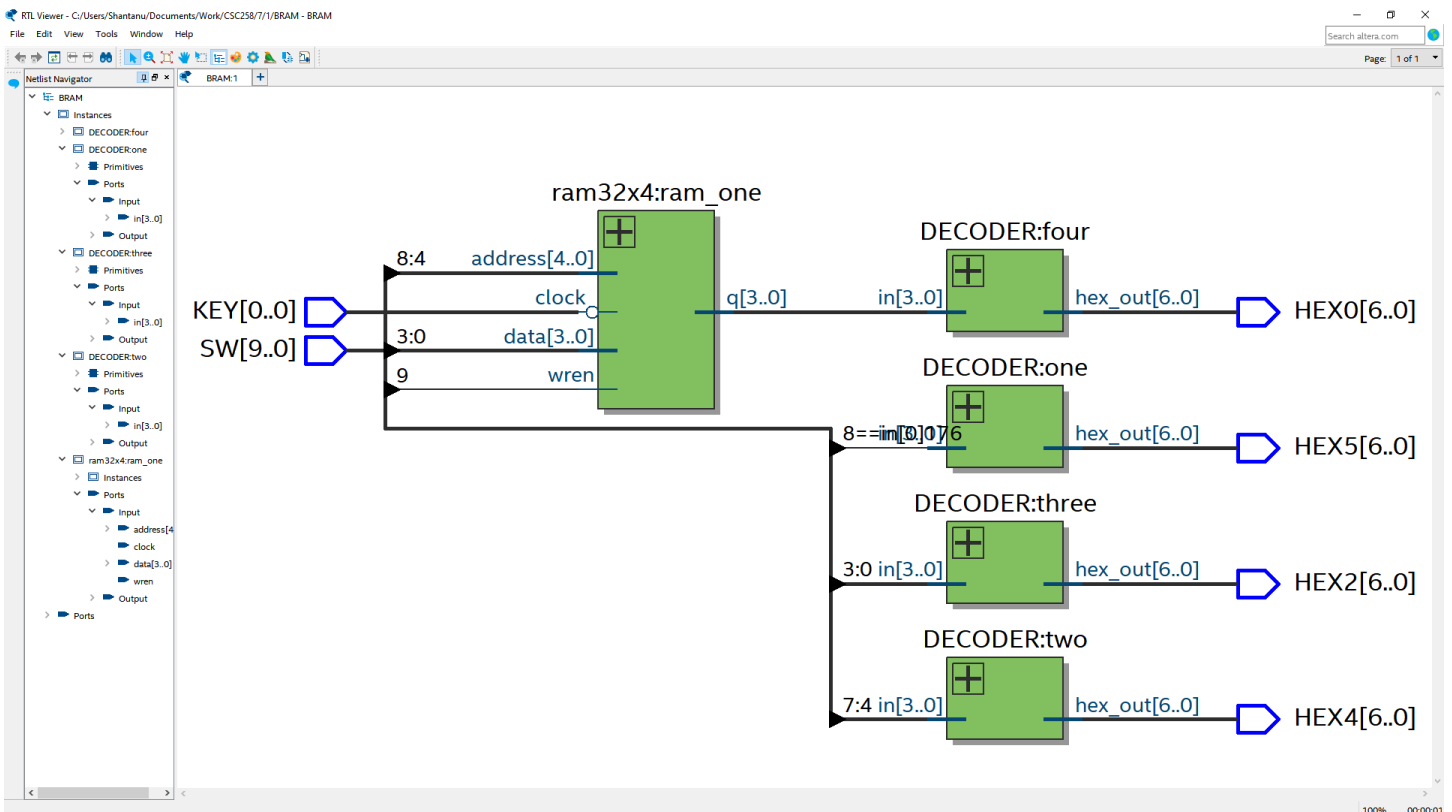


Part 2

  
1. Draw the Schematics and Post Screenshots – Please see module datapath of part2.v



 2. Design the FSM and simulate it and Post Screenshots – Please see module control of part2.v



State	LOAD_X	LOAD_Y	LOAD_C	plot
X_L	1	0	0	0
Y_L_C	1	1	1	0
d	1	1	1	1

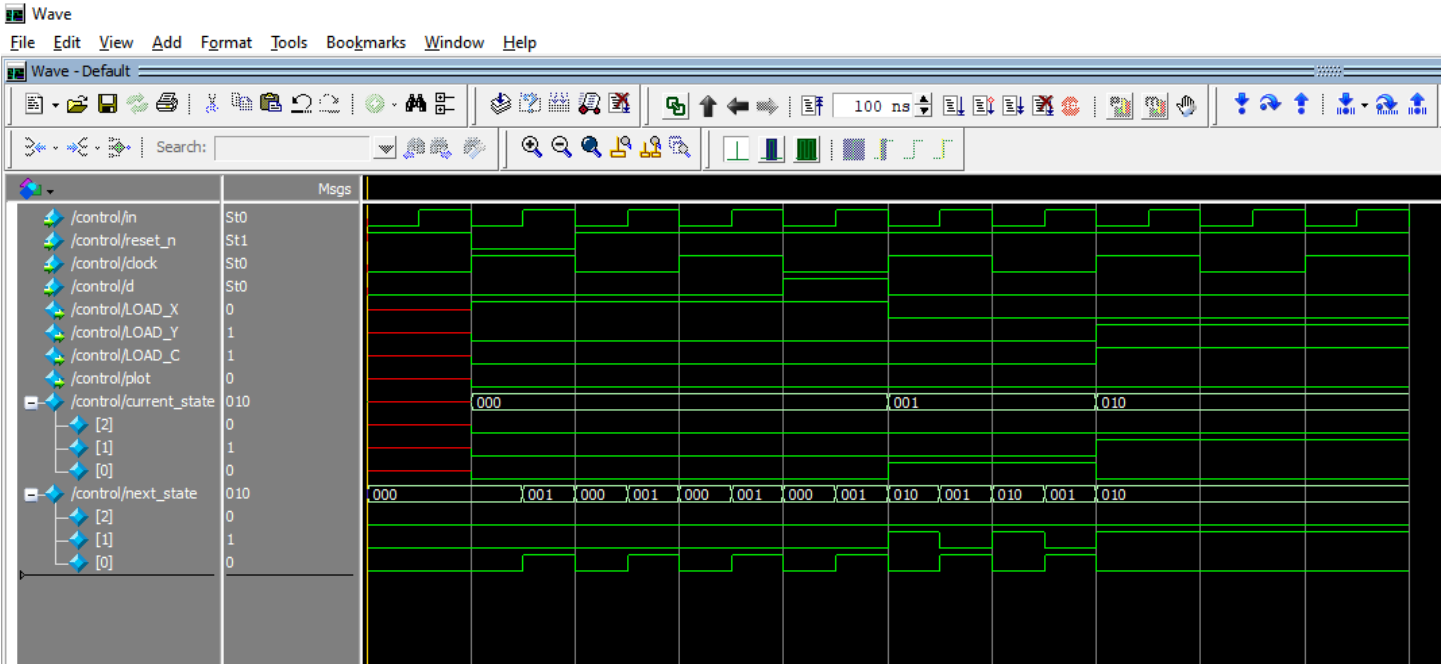

3. Simulate and Post Screenshots – Please see module joined of part2.v

