

LAB 6

Part I

2. Is resetn synchronous or asynchronous?

Ans – The resetn signal is a synchronous reset. It has an active low. To reset the FSM to the starting state, the clock has to be set to high whenever we want to reset it.


3. Complete the State Table and Show the Code

Ans – For the completed code, please refer to sequence_detector.v

| Current State | Switch Input | Output State |
|---------------|--------------|--------------|
| 000 | 0 | 000 |
| 000 | 1 | 001 |
| 001 | 0 | 000 |
| 001 | 1 | 010 |
| 010 | 0 | 100 |
| 010 | 1 | 011 |
| 011 | 0 | 110 |
| 011 | 1 | 101 |
| 100 | 0 | 000 |
| 100 | 1 | 110 |
| 101 | 0 | 100 |
| 101 | 1 | 101 |
| 110 | 0 | 000 |
| 110 | 1 | 010 |

Note: One's marked in yellow output the result (ie. 1)

4. Simulate the circuit and post screenshots –

 


Part II

2. Draw a table that shows the state of the Registers and control signals for each cycle of your computation

| Cycle | Value | Alu_select_a | Alu_select_b | B | R |
|-------|-----------------------|--------------|--------------|-------------------|-----------------------|
| 0 | $A * X$ | 00 | 11 | B | - |
| 1 | $A * X + B$ | 00 | 01 | $A * X + B$ | - |
| 2 | $X * (A * X + B)$ | 11 | 01 | $X * (A * X + B)$ | - |
| 3 | $X * (A * X + B) + C$ | 01 | 10 | $X * (A * X + B)$ | $X * (A * X + B) + C$ |

 3. Draw a state diagram for your controller starting with the register load states provided in the example FSM



4. Modify the provided FSM code to implement your controller and synthesize it. You should only modify the control module.

Ans – Please check poly_function.v

6. Simulate the circuit and post screenshots –

