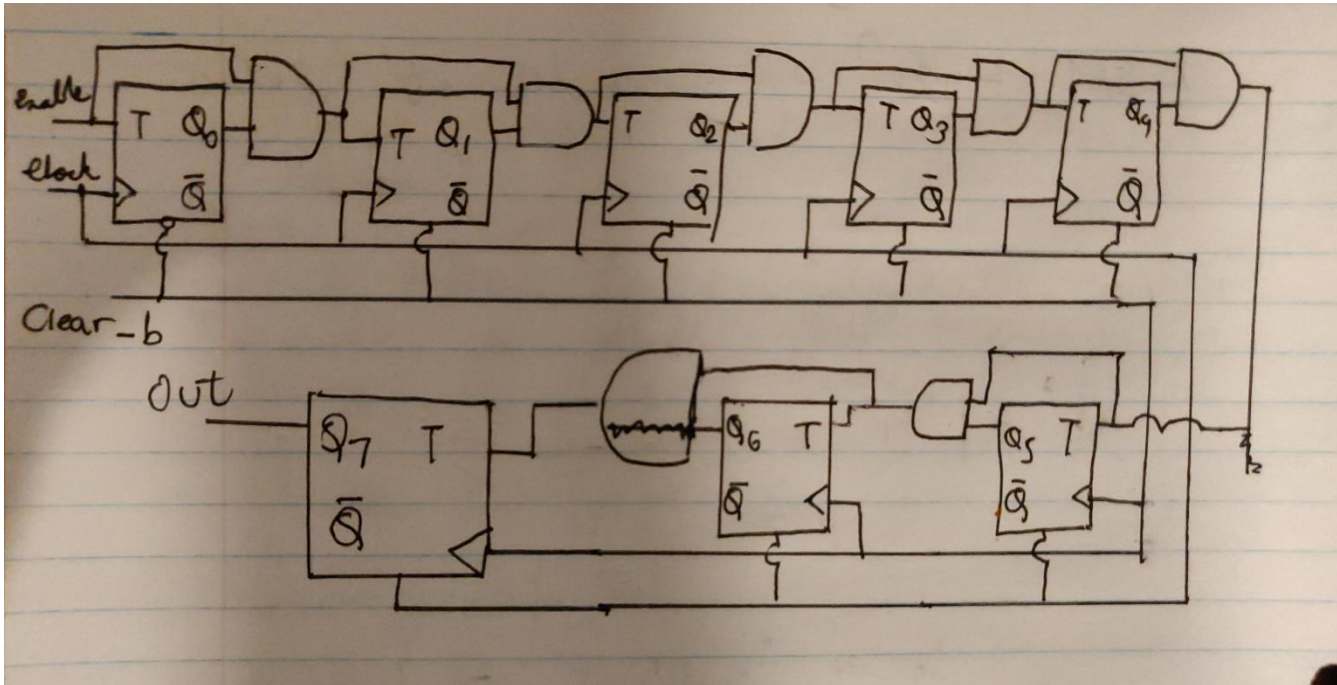


LAB 5


Part I

1 & 2




3. Verilog Code – Please check counter.v

4. *Simulate the circuit –*

 

5. *Simulate the circuit again –*

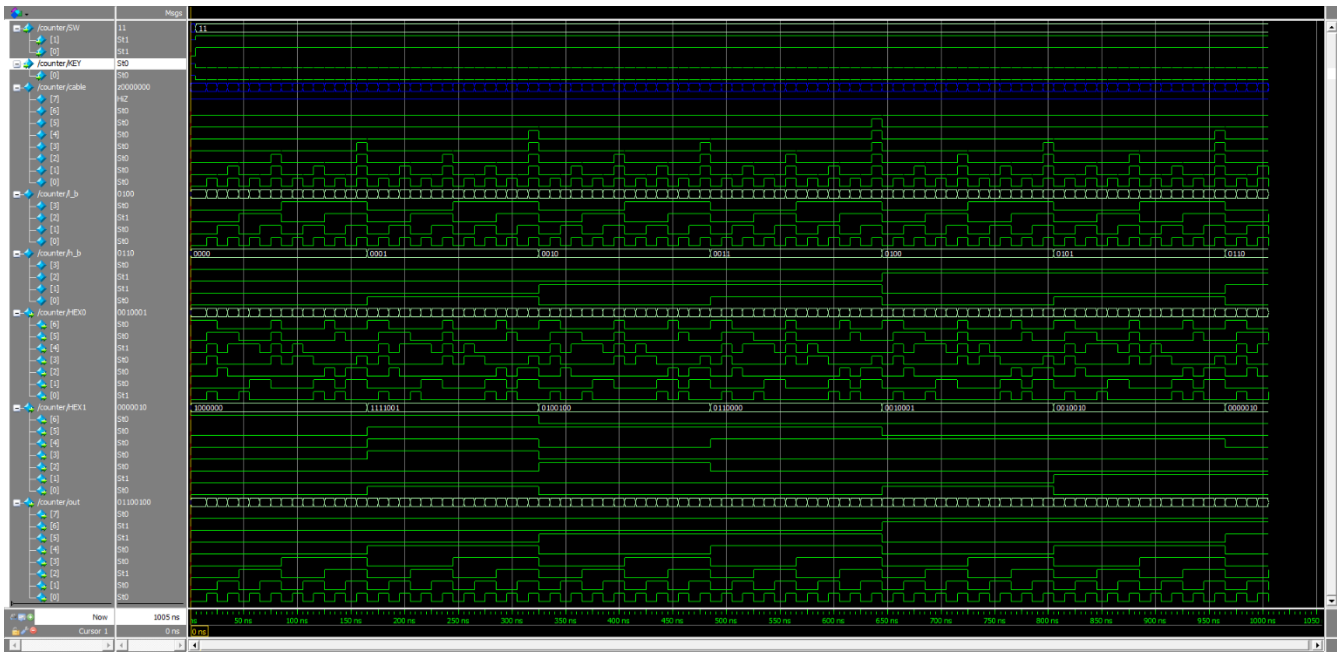

6. Create a new Quartus Project –


Logic utilization (in ALMs)	13 / 32,070 (< 1 %)
A. Total registers	8

Slow 1100mV 85C Model Fmax Summary

<<Filter>>

	Fmax	Restricted Fmax	Clock Name	Note
B. 1	666.67 MHz	621.89 MHz	KEY[0]	limit due to low minimum pulse width violation (tcl)

7. View the Synthesized Circuit.

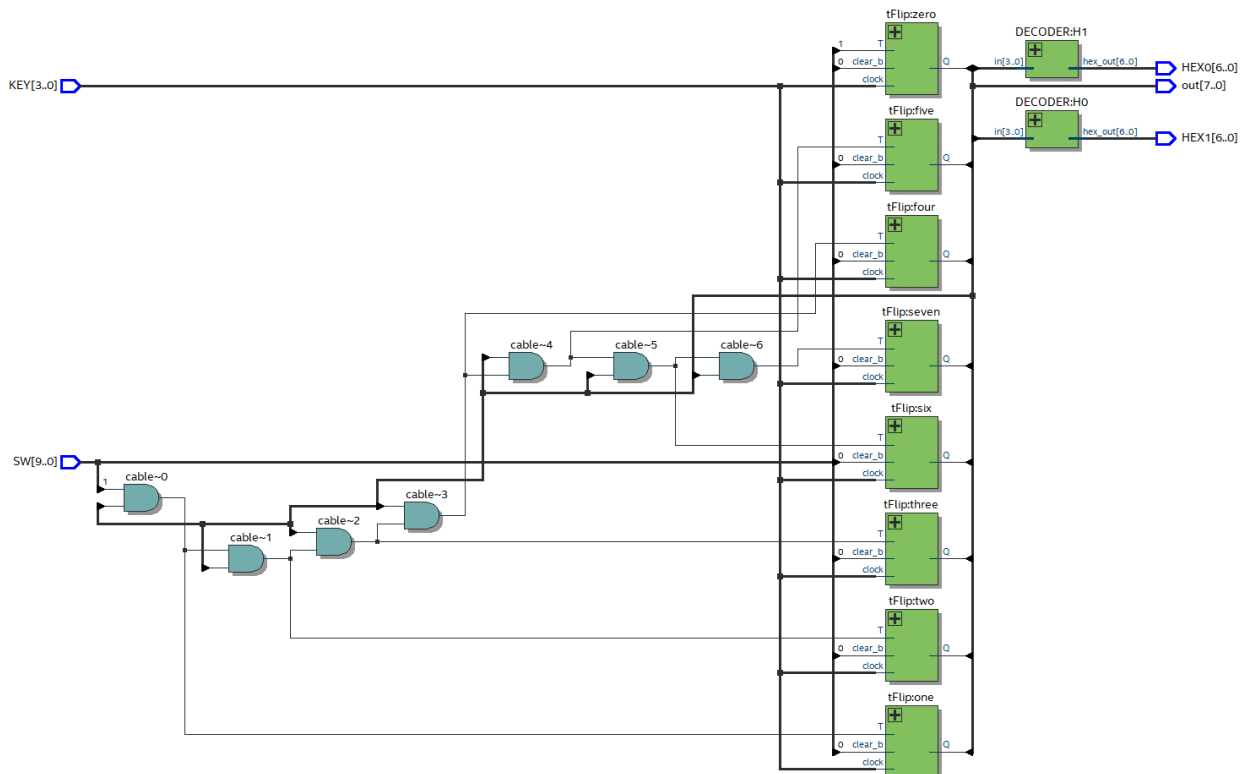

Part II

A1. Since it is 4 bits only, adding 1 to 1111 will make it 0000 and we are back to the default position.


A2. Since 9 is 1001 in binary, we change `if (q == 4'b1111)` to `if (q == 4'b1001)`

A3. At this speed we will see all the numbers flashing 50 Million times a second. Due to our persistence of vision, being 10 Hz we will see 8

A4. We should require not more than 2 counters


A5. Since $2^{26} = 67108864$, it will require 26 – bits minimum

1.

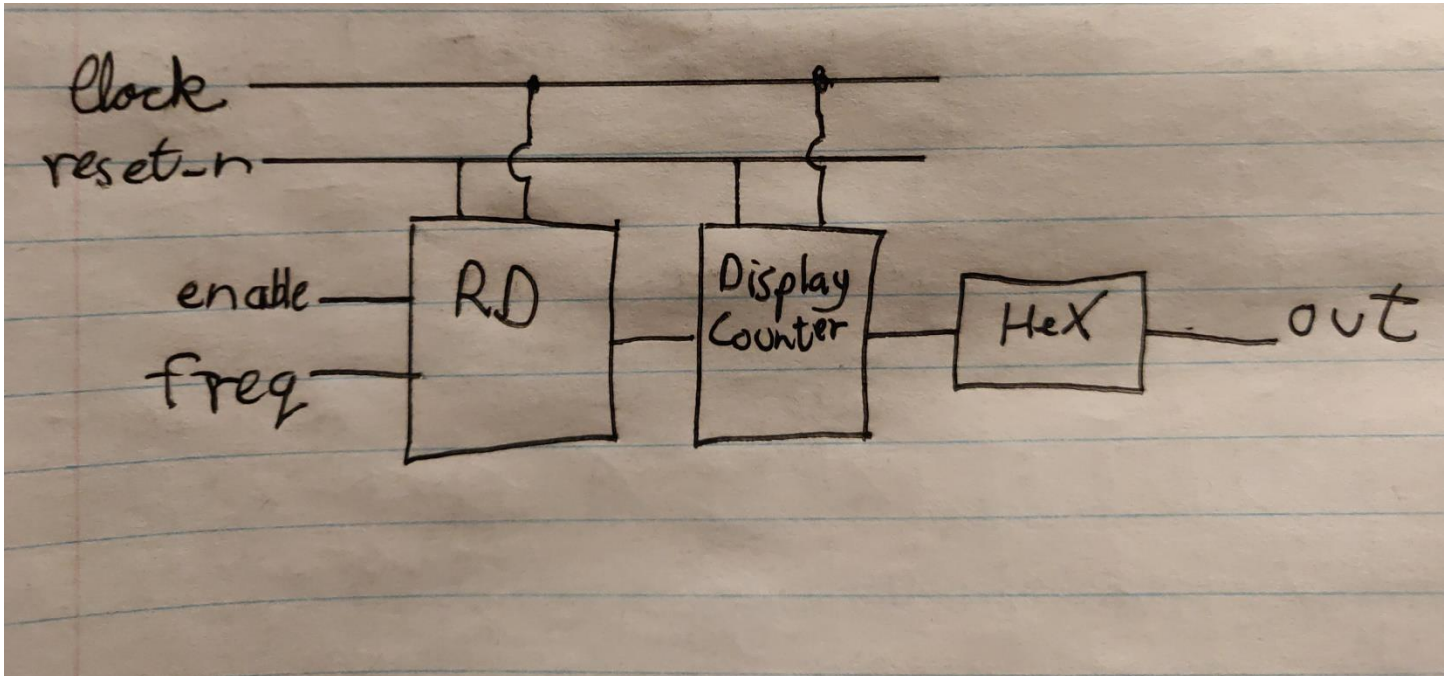

2. Verilog Code – Please check `clk.v`

3. Simulate the circuit –

 


Part III

1.

Letter	Morse Code	Pattern Representation (pattern length is <u>14</u> bits)
S	• • •	10101 000 000 000
T	—	11100000000000
U	• • —	10101110000000
V	• • • —	10101011100000
W	• — —	101110111100000
X	— • • —	111010101110
Y	— • — —	11101011101110
Z	— — • •	11101110101000

2.

 

3. Verilog Code – Please check morse.v

4. Screenshot of the Simulations –

